

AQA (Trilogy) Combined Science


GCSE Unit 6.2 Electricity -


Answers

Test (Levels 4 – 9)

1.		(4 marks total)
a.	lamp fuse  LDR thermistor diode one mark per correct answer maximum 3	(3 mark)
b.	Delocalised electrons	(1 mark)
2.		(7 marks total)
a.	Total power = $500+1500+1600+2500+700 = 6800$ watts Current = $6800 \div 230$ = 29.57 A (2dp) - (accept 29.565) This is less than 30A so it is safe to use Maximum 1 mark for an unqualified yes Maximum 2 marks for 29.57 with no working or qualifying yes	(1 mark) (1 mark) (1 mark) (1 mark)
b.	Q=Ixt so, $2400 = I \times 150$ $I = 2400/150 = 16$ unit = amps Allow 1 mark for correct substitution but no answer	(1 mark) (1 mark) (1 mark)
3.		(6 marks total)
a.	V=IR or potential difference = current x resistance	(1 mark)
b.	$3.6 = 0.17 \times R$ $R = 3.6 \div 0.17$ $R = 21.18$ (2dp) - allow 21 or 21.2 Allow answer showing no working out for 3 marks	(1 mark) (1 mark) (1 mark)

c.	As resistance increases, current decreases... ...this makes the bulb dimmer Accept opposite argument	(1 mark) (1 mark)
----	---	----------------------

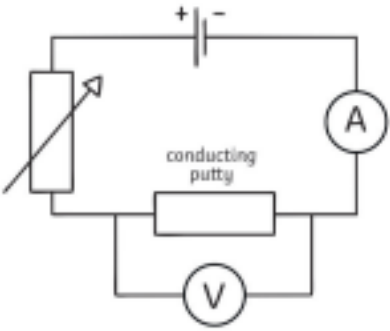4.		(9 marks total)
a.		(2 marks)
b.	A variable resistor can be added Accept change resistance, or Change number of cells/batteries Accept alter voltage/potential difference	(1 mark) (1 mark)
c.	0.24 (Ω)	(1 mark)
d.	$V=IR$ so $V = 0.15 \times 0.24 = 0.036$ (v) Allow 1 mark for correct substitution without answer Allow 2 marks if correct calculation with the incorrect answer from c. ecf	(1 mark) (1 mark)
e.	As the putty gets thicker, the resistance increases (or reverse)	(1 mark)
f.	Any one from: Inaccurate measurements of current/length/voltage Putty not the same thickness throughout the cylinder Accept sensible qualified systematic or human errors	(1 mark)
5.		(4 marks total)
a.	The voltage across the cables is increased This decreases the current (through the cables) To reduce heat energy loss in the wires	(1 mark) (1 mark) (1 mark)
b.	Reduces the voltage to allow safe domestic use	(1 mark)

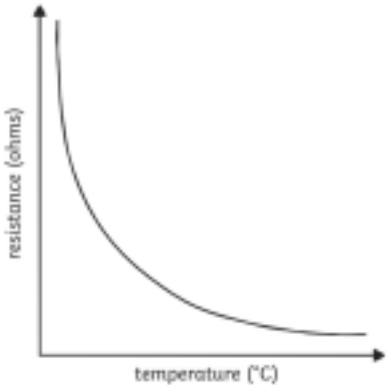6.		(7 marks total)
a.	Series circuits have components in a loop, parallel circuits are branched Allow brighter bulbs than a series circuit	(1 mark)
b.	Parallel circuits allow independent switching Allow: brighter bulbs than in a series circuit or if one bulb blows the rest stay on	(1 mark)
c.	Fuse	(1 mark)
d.	A - same as/less than	(1 mark)
e.	Current is continuously... ...changing direction	(1 mark) (1 mark)
f.	50Hz	(1 mark)
7.		(3 mark total)
a.	A circuit which automatically turns a heating system on and off	(1 mark)
b.		(1 mark)
c.		(1 mark)

8.		(10 marks total)
----	--	------------------

a.	Component C is a variable resistor and will allow a range of Potential difference values to be obtained Accept will increase/decrease the current/voltage/pd/resistance Accept control or change Both parts needed for full mark	(1 mark)
b.	The bulb gets hotter/temperature of the bulb increases	(1 mark)
c.	Power = pd x current (or $P=VI$) So, $9 \times 2.5 = 22.5$ Watts (W)	(1 mark) (1 mark)
d.	QWC 5-6 marks shows a detailed comparison of both cost and energy efficiency 3-4 marks shows a clear comparison of cost OR energy efficiency 1-2 marks shows a basic comparison of an aspect of either cost OR energy efficiency Examples Energy efficiency LED has same output but less power LED is 22% more efficient LES has less wasted energy LED uses a smaller current LED produces less heat Cost LED is approximately 6 times more expensive LED cheaper to run than a halogen 18 halogens needed to last the same amount of time as one LED 18 halogens cost £36,90	(6 marks)